

# Digital Logic

## Day 1

[uarch.space](https://uarch.space)

[uarch.space/slides/day1.pdf](https://uarch.space/slides/day1.pdf)

# Wires


- Click and drag to move camera.
- Scroll or press +/- to zoom in and out.




Sets the power connected wires




Reads the power of connected wires

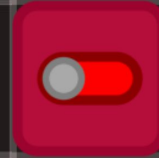

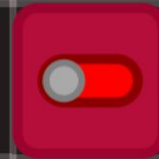

click and drag to create wire

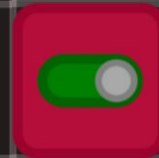


click to toggle switch on


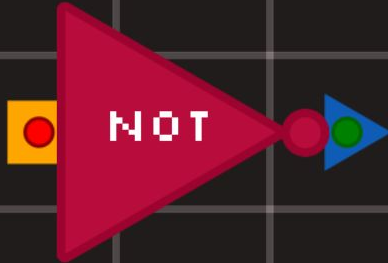
# NOT GATE

A NOT gate has one input  and one output . It inverts the signal that it gets.





We can represent this with a truth table.


The A column represents the input; the Y column the corresponding output.







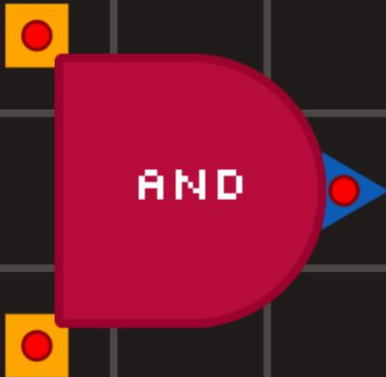
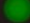




A	Y
	
	

*try all possible input combinations to continue*

# AND GATE

A AND gate has two inputs  and one output . It is on only when both inputs are on.





A	B	Y
		
		
		
		


You can delete gates and wires by right clicking.


now you try











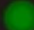

# NAND GATE

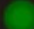A NAND gate has two inputs  and one output . It is same as AND, but the output is always inverted.

It's like an AND gate with a NOT gate on the end.



In this level you need to make your own gate. Your switch blocks have been replaced by INPUT blocks. Click the  icon to place components down.

Click the play  button to run the tests. If your circuit is correct, it should pass 4/4 tests.

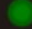

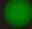









A	B	Y
		
		
		
		

*now you try*

# OR GATE

An OR gate has two inputs  and one output . It is on if at least one of the inputs is on.

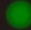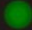You can move gates by clicking and dragging.

A	B	Y
		
		
		
		

Hint:

What does the truth table look like if you invert every value?

*now you try*


# NOR GATE




Just like NAND is AND but the output is inverted, NOR is OR, but the output is inverted.

Try to see how few gates you can use for this one!

A	B	Y
●	●	●
●	●	●
●	●	●
●	●	●
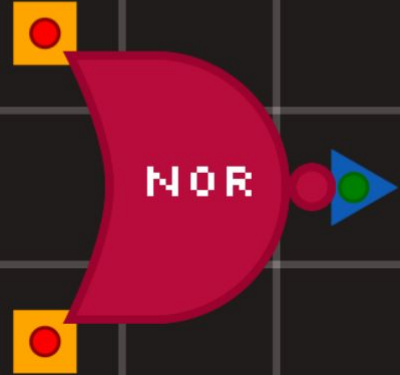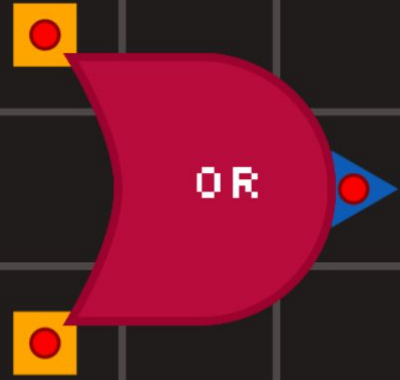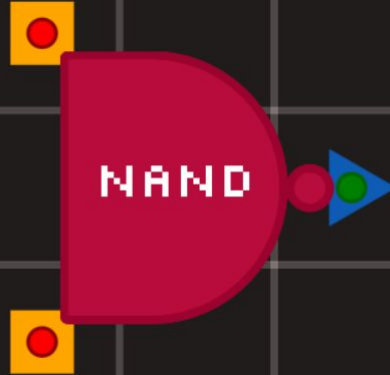
# Challenges

- All of the gates you have made are unlocked now in the  menu.
- Some of these gates are enough to make the rest of the gates. Which are they?
- What is De Morgan's laws and how do they apply here?





# Solutions:

[uarch.space/solutions/day1.pdf](https://uarch.space/solutions/day1.pdf)