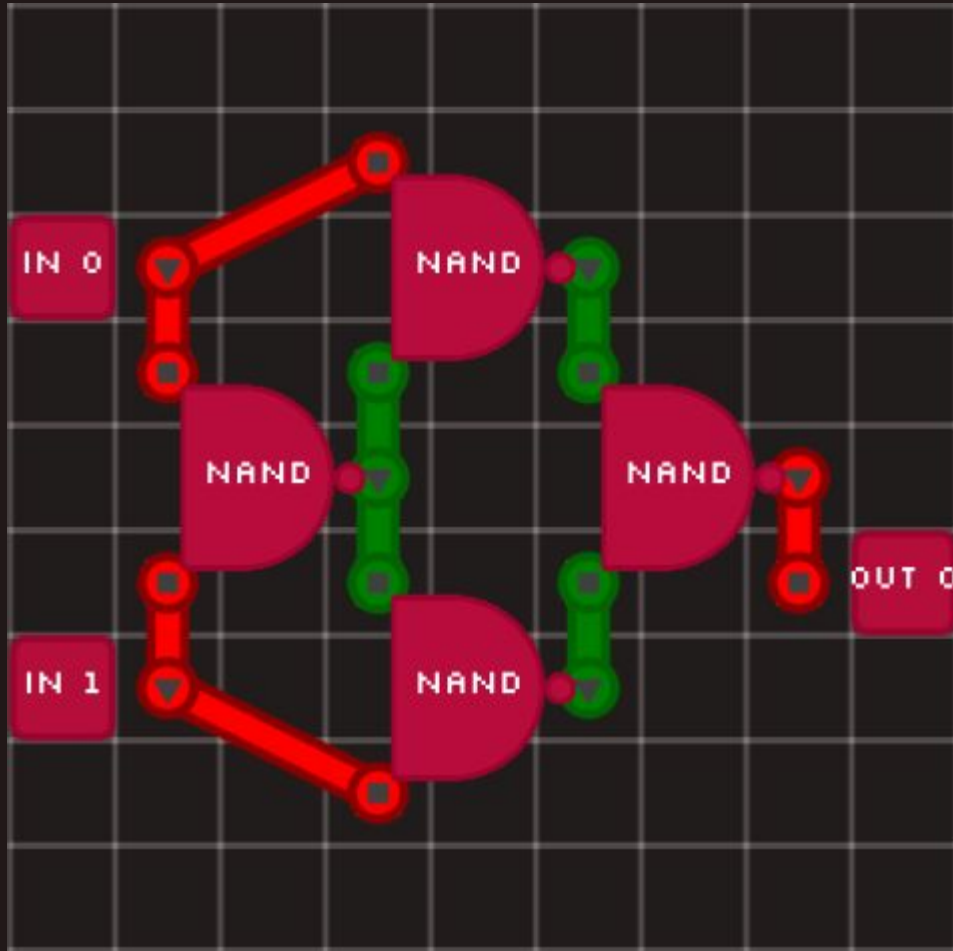


Day 2


Solutions

XOR GATE



There are many varied ways to solve this one. Here is a NAND only solution

XNOR GATE

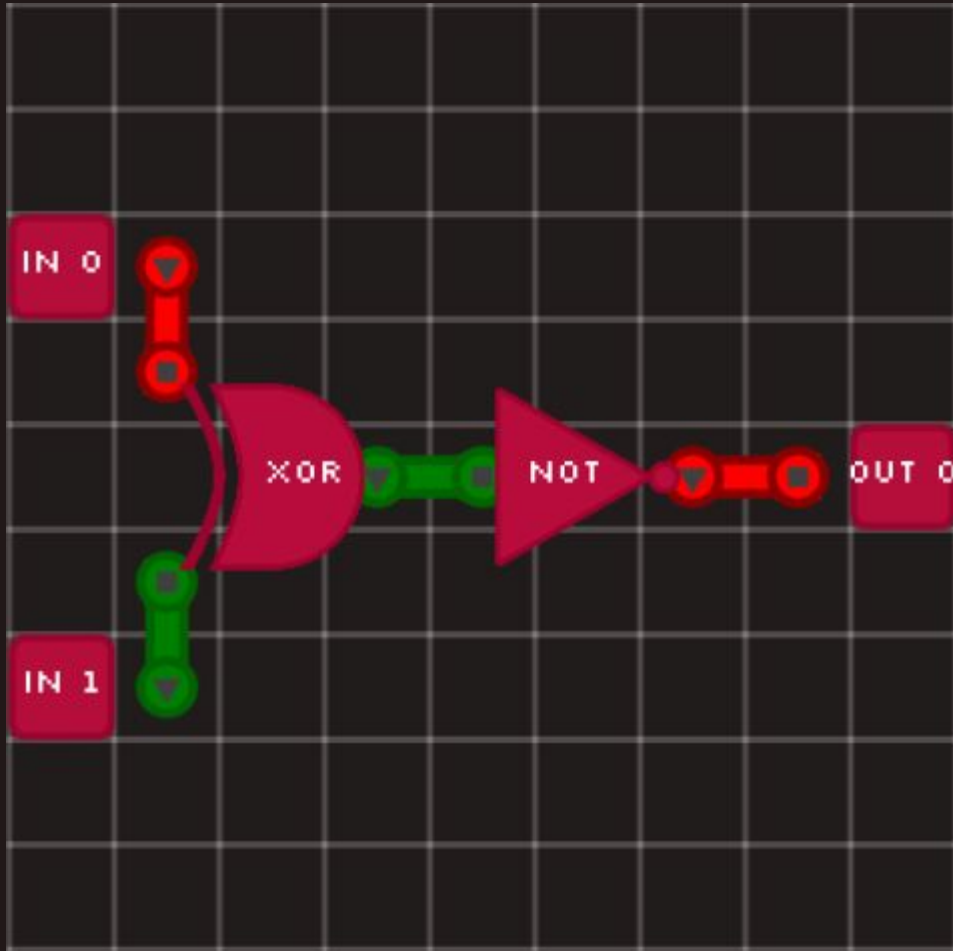

Challenges

Note that a single XOR gate is enough to be on only if an odd number of inputs are on. We can stack XOR gates to make a “mega-XOR” gate.

